

**DEPARTMENT OF
ELECTRONICS & COMMUNICATION ENGINEERING**

VLSI DESIGN LAB MANUAL

PVP20 REGULATIONS

III B.TECH II SEM



PRASAD V POTLURI SIDDHARTHA INSTITUTE OF TECHNOLOGY

(Autonomous, Accredited by NBA & NAAC, an ISO 9001:2015 certified institution)

(Sponsored by Siddhartha Academy of General & Technical Education)

VIJAYAWADA – 520 007


EXPERIMENT 1

CMOS Inverter

AIM: To Design and simulate CMOS Inverter using VLSI CAD tools.

APPARATUS: PC loaded with VLSI CAD tools


Schematic:

 

Input	Output
1	0
0	1

Truth table

Model waveform:

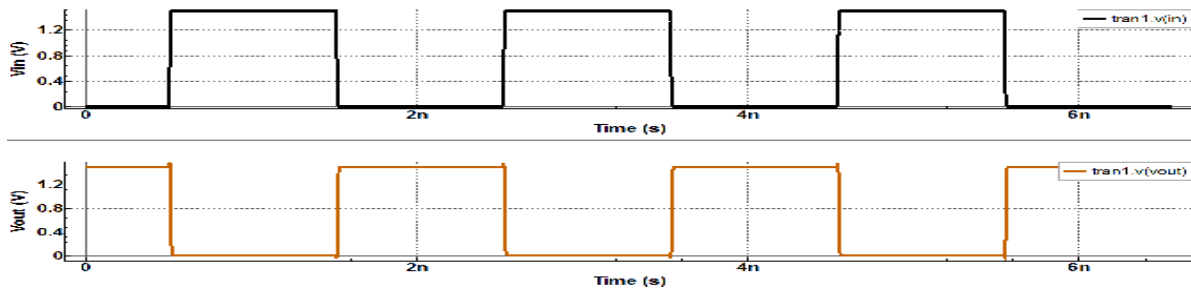

Procedure:


1. Open the VLSI CAD tool software.
2. Construct the circuit
3. Observe the output waveforms VLSI CAD tool software

Result:


EXPERIMENT 2

COMMON SOURCE AMPLIFIER

Schematic

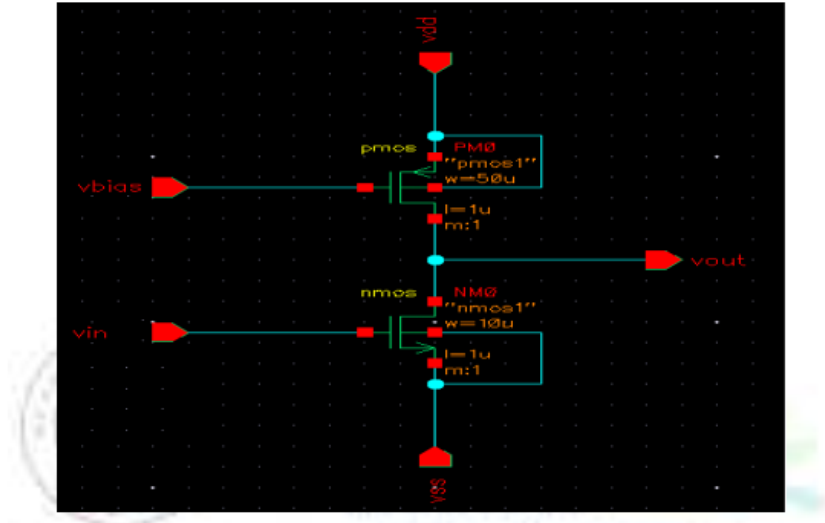

Model wave form

 

Procedure:


1. Open the VLSI CAD tool software.
2. Construct the circuit
3. Observe the output waveforms VLSI CAD tool software

Result:


EXPERIMENT 3

COMMON DRAIN AMPLIFIER

Schematic Capture

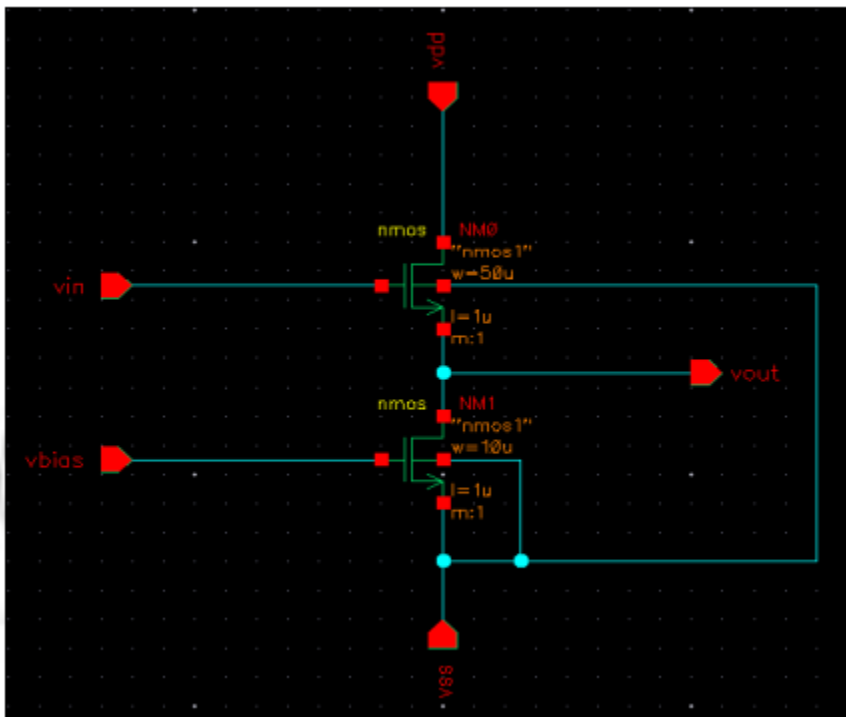

Model wave form

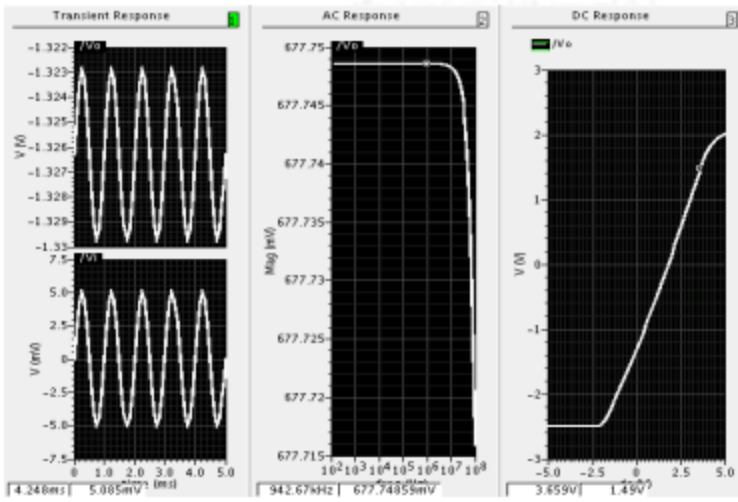

Procedure:

1. Open the VLSI CAD tool software.
2. Construct the circuit
3. Observe the output waveforms VLSI CAD tool software

Result:



EXPERIMENT 4

DECODER

AIM: To Design and simulate decoder using VLSI CAD tools.

APPARATUS: PC loaded with VLSI CAD tools


Schematic:

  

Truth table:

A	D ₁	D ₀
0	0	1
1	1	0

Model Wave forms:

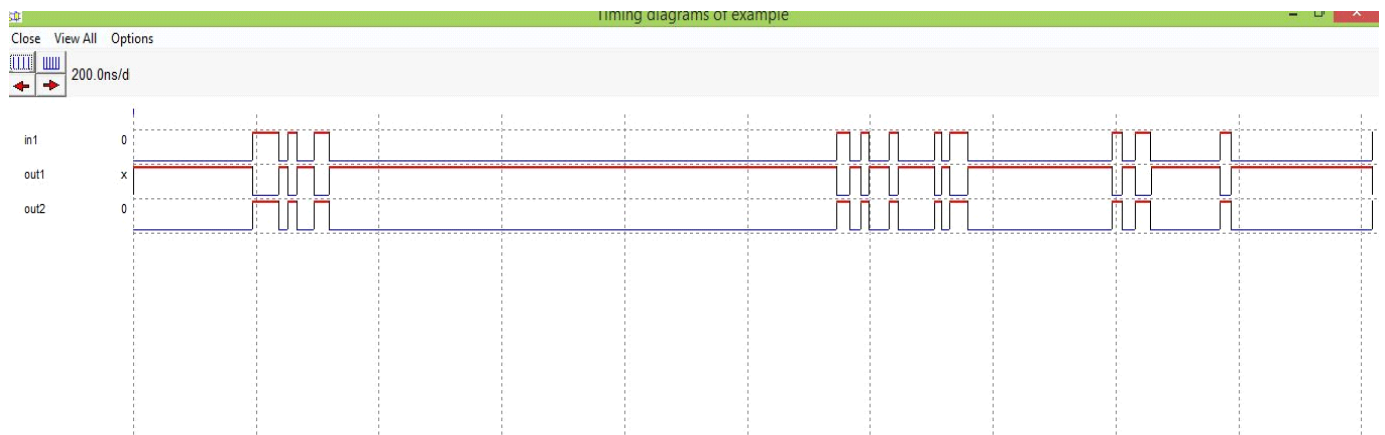

Procedure:

4. Open the VLSI CAD tool software.
5. Construct the circuit
6. Observe the output waveforms VLSI CAD tool software

Result:

EXPERIMENT 5


Basic GATES

AIM: To Design and simulate gates using VLSI CAD tools.

APPARATUS: PC loaded with VLSI CAD tools

Schematic:

AND gate:

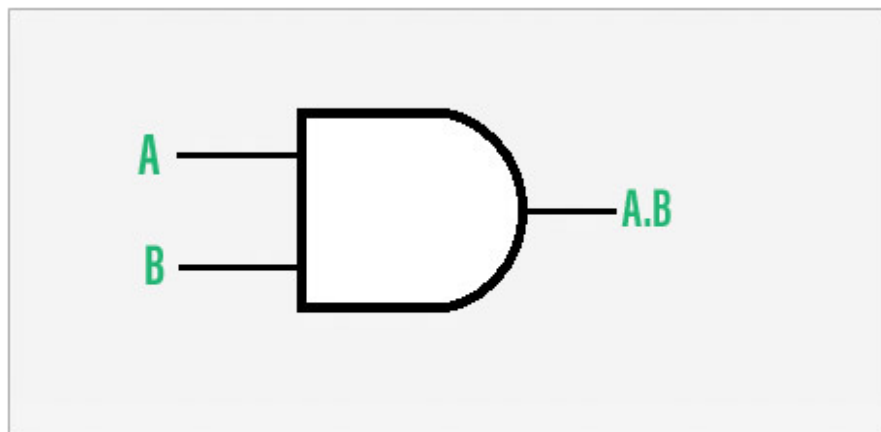


Symbol of Two-Input AND Gate

Truth table:


Input		Output
A	B	A AND B
0	0	0
0	1	0
1	0	0
1	1	1

Model waveforms

 

OR gate:

Schematic:

 


Symbol of Two-Input OR Gate

Truth table:

Input		Output
A	B	A OR B
0	0	0
0	1	1
1	0	1
1	1	1

Model Wave forms:

 

Procedure:

1. Open the VLSI CAD tool software.
2. Construct the circuit
3. Observe the output waveforms VLSI CAD tool software

Result:

EXPERIMENT 6

Universal GATES

AIM: To Design and simulate universal gates using VLSI CAD tools.

APPARATUS: PC loaded with VLSI CAD tools

NAND gate:

Schematic




Symbol of NAND Gate

Truth table:


Input		Output
A	B	A NAND B
0	0	1
0	1	1
1	0	1
1	1	0

Model wave forms:

 

NOR gate:

Schematic:

 


Symbol of the NOR Gate

Truth table:

A	B	A NOR B
0	0	1
0	1	0
1	0	0
1	1	0

Model Wave forms:

 

Procedure:

1. Open the VLSI CAD tool software.
2. Construct the circuit
3. Observe the output waveforms VLSI CAD tool software

Result:


EXPERIMENT 7

PRIORITY ENCODER

AIM: To Design and simulate Priority Encoder using VLSI CAD tools.

APPARATUS: PC loaded with VLSI CAD tools

Schematic:

 

Logic Equations:

$$A = D3 + D1D2'$$

$$B = D2 + D3$$

$$V = D0 + D1 + D2 + D3$$

Truth table:

Procedure:

1. Open the VLSI CAD tool software.
2. Construct the circuit
3. Observe the output waveforms VLSI CAD tool software

Result:


EXPERIMENT 8

MULTIPLEXER


AIM: To Design and simulate multiplexer using VLSI CAD tools.

APPARATUS: PC loaded with VLSI CAD tools


Schematic:

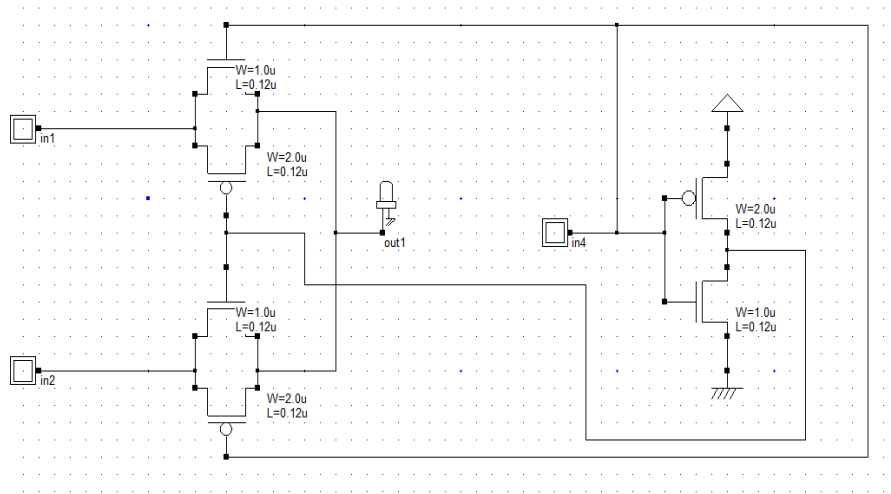

Logicdiagram

 

Truth Table:

 

A	B	S	Out
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

(c)

Procedure:

4. Open the VLSI CAD tool software.
5. Construct the circuit
6. Observe the output waveforms VLSI CAD tool software

S	Out
0	B
1	A

(b)

Result:


EXPERIMENT 9

HALF ADDER

AIM: To Design and simulate Half Adder using VLSI CAD tools.

APPARATUS: PC loaded with VLSI CAD tools


Schematic:

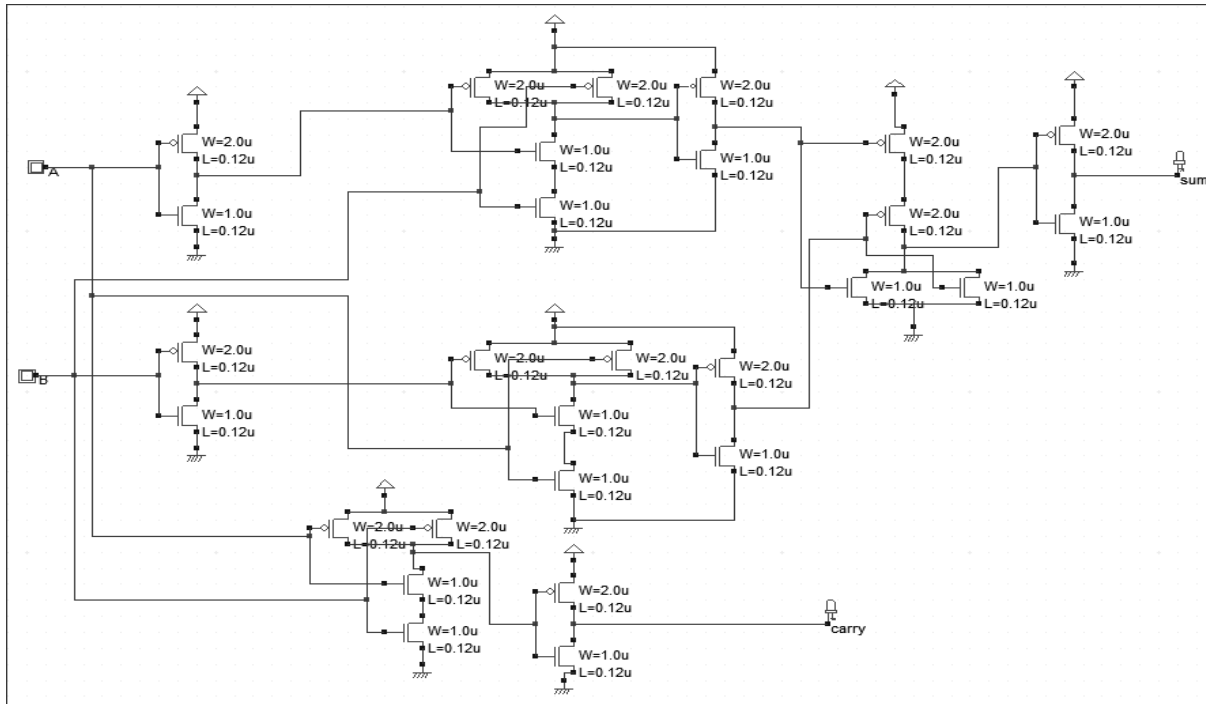

Truth table:

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


Logic Diagram:

 

Sum = A XOR B

Carry = A AND B

Model Waveforms:

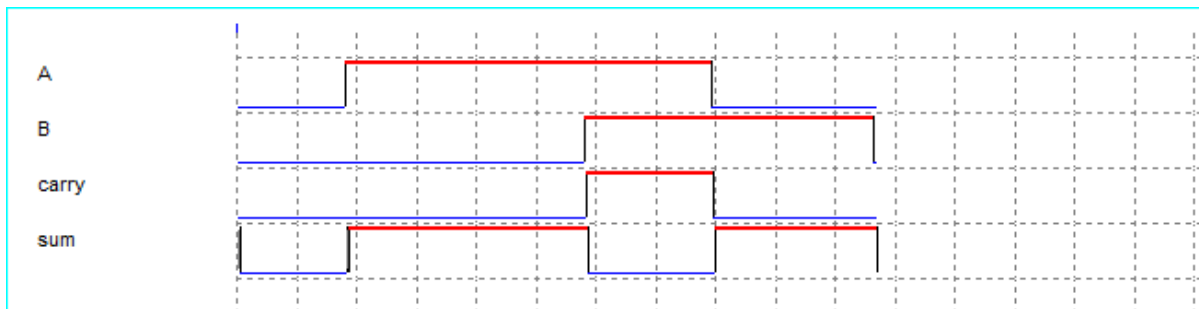

Procedure:

1. Open the VLSI CAD tool software.
2. Construct the circuit
3. Observe the output waveforms VLSI CAD tool software

Result:


EXPERIMENT 10

COMPARATOR

AIM: To Design and simulate Comparator VLSI CAD tools.

APPARATUS: PC loaded with VLSI CAD tools


Schematic:

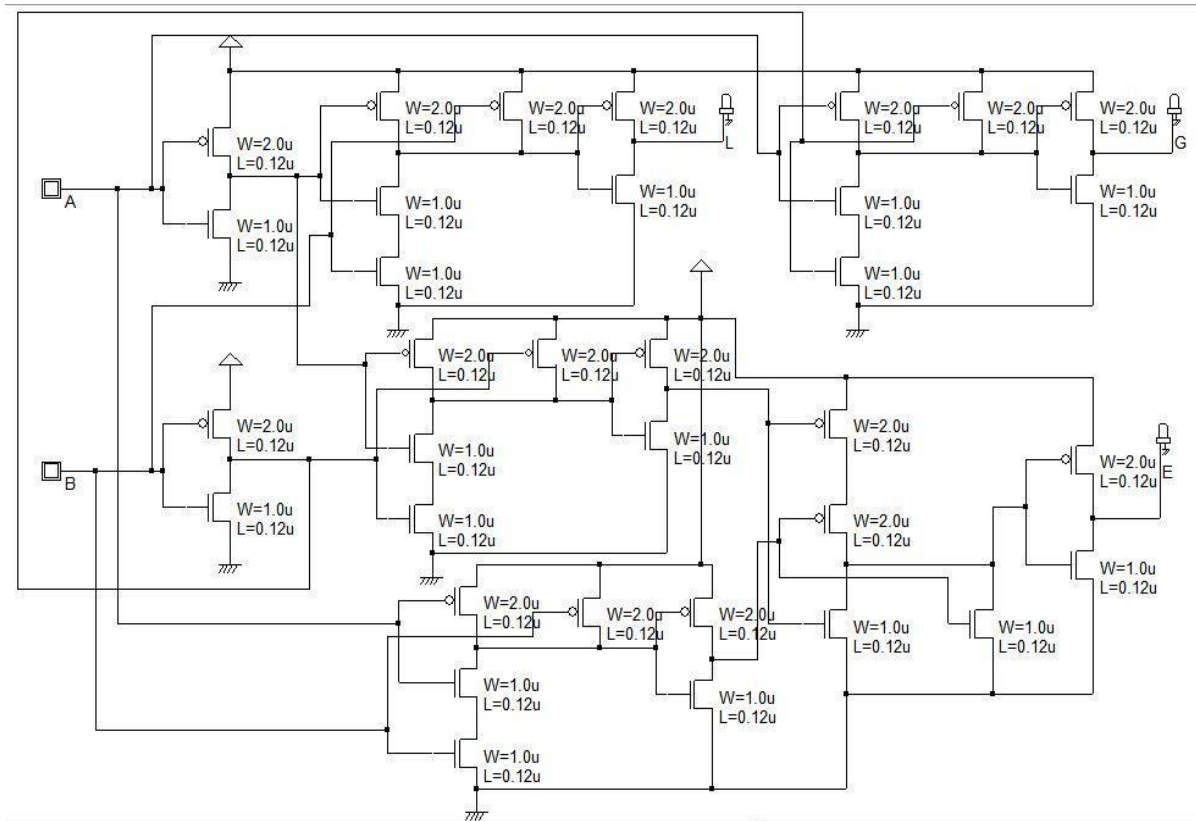

Truth table:

A	B	A<B	A=B	A>B
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

Logic diagram:

 


equations

$$A > B = AB'$$

$$A < B = A'B$$

$$A = B = A'B' + AB$$

Model Waveforms:

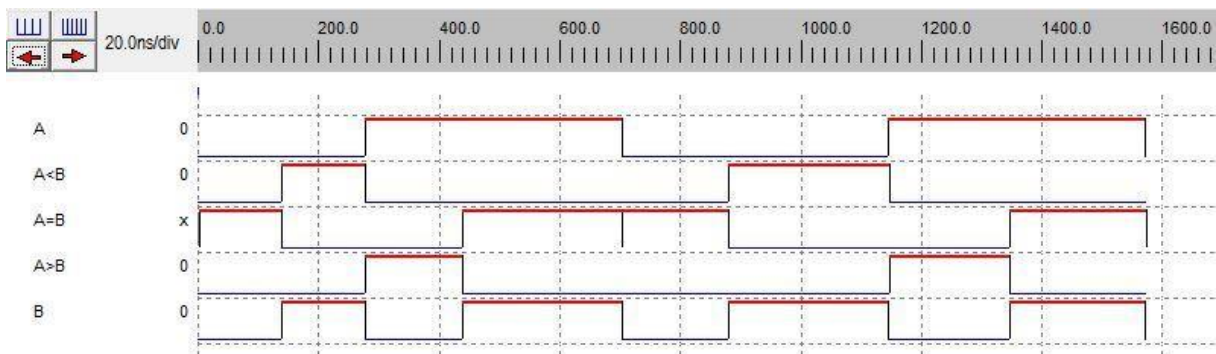

Procedure:

1. Open the VLSI CAD tool software.
2. Construct the circuit
3. Observe the output waveforms VLSI CAD tool software

Result: