

Code: 23EE3301

II B.Tech - I Semester – Regular / Supplementary Examinations
NOVEMBER 2025

ELECTRICAL CIRCUIT ANALYSIS - II
(ELECTRICAL & ELECTRONICS ENGINEERING)

Duration: 3 hours

Max. Marks: 70

-
- Note: 1. This question paper contains two Parts A and B.
 2. Part-A contains 10 short answer questions. Each Question carries 2 Marks.
 3. Part-B contains 5 essay questions with an internal choice from each unit. Each Question carries 10 marks.
 4. All parts of Question paper must be answered in one place.

BL – Blooms Level

CO – Course Outcome

PART – A

		BL	CO
1.a)	How do you find the average and RMS values of a non-sinusoidal periodic waveform using Fourier coefficients?	L2	CO1
b)	What is the relationship between the trigonometric and exponential forms of a Fourier series?	L2	CO1
c)	Express the relationship between Z and Hybrid (h) parameters.	L2	CO2
d)	Why h-parameters are called as 'hybrid' parameters?	L2	CO2
e)	Distinguish between the natural response and the forced response of a circuit.	L2	CO3
f)	What is the condition for a series RLC circuit to be underdamped, overdamped and critically damped?	L2	CO3
g)	List the advantages of a three-phase system over a single-phase system.	L2	CO4
h)	How can the power factor of a balanced three-phase load be determined from the readings of two watt meters?	L2	CO4
i)	Define the cut-off frequency for a filter.	L1	CO5

j)	Draw the equivalent circuit of a typical band-pass filter.	L3	CO5
----	--	----	-----

PART – B

		BL	CO	Max. Marks
--	--	----	----	------------


UNIT-I

2	Solve the Laplace transform of the following functions: a) $f(t)=e^{-at} \sin(\omega t)$ b) $f(t)=t^2 u(t-1)$	L3	CO1	10 M
---	---	----	-----	------

OR

3	Determine the Laplace transform of the periodic sawtooth waveform.	L3	CO1	10 M
---	--	----	-----	------

UNIT-II

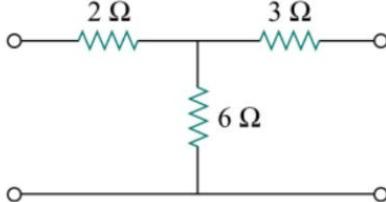4	Find the z-parameters of the two-port network shown in the figure.	L3	CO2	10 M
				

OR

5	a)	Derive the expressions for converting Y-parameters into ABCD (transmission) parameters.	L3	CO2	5 M
	b)	Determine the transmission parameters for a two-port network, Given Z-parameters are $Z = \begin{bmatrix} 10 & 5 \\ 3 & 8 \end{bmatrix}$.	L3	CO2	5 M

UNIT-III

6	A series RLC circuit with $R=5 \Omega$, $L=1 \text{ H}$ and $C=0.25 \mu\text{F}$ is excited by a 100 V DC source at $t=0$. Obtain the expression for the current $i(t)$ using the Laplace transform approach.	L4	CO3	10 M
---	---	----	-----	------

OR

7	a)	Develop an expression for the step response of a series R-C circuit.	L4	CO3	5 M
	b)	Derive the general expression for the current response of a series R-L circuit excited by a sinusoidal voltage source, $V = V_m \sin(\omega t + \theta)$.	L4	CO3	5 M

UNIT-IV

8	a)	Derive the relationship between line currents and phase currents in a star -connected three-phase balanced system.	L3	CO4	5 M
	b)	The two-wattmeter method produces readings of 1500 W and 750 W when connected to a delta-connected load. Calculate the total active power, total reactive power and the power factor of the load.	L3	CO4	5 M

OR

9	A balanced star-connected load with an impedance of $(12 + j15) \Omega$ per phase is connected to a three-phase, 400 V, 50 Hz supply. Determine the line currents, power factor and total active power consumed by the load.			L4	CO4	10 M

UNIT-V

10	a)	Design a constant-k high-pass T-section and π -section filter with a cut-off frequency of 3000 Hz and a nominal characteristic impedance of 500Ω .	L4	CO5	5 M
	b)	Explain the characteristics of a Constant-K high-pass filter with a neat diagram.	L3	CO5	5 M

OR

11	Design a constant-k low pass filter having cut-off frequency of 4000 Hz and a nominal characteristic impedance of 500Ω .			L4	CO5	10 M