

Code: 23EE3301

**II B.Tech - I Semester – Regular / Supplementary Examinations
NOVEMBER 2025**

**ELECTRICAL CIRCUIT ANALYSIS - II
(ELECTRICAL & ELECTRONICS ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

Note: 1. This question paper contains two Parts A and B.

2. Part-A contains 10 short answer questions. Each Question carries 2 Marks.

3. Part-B contains 5 essay questions with an internal choice from each unit. Each Question carries 10 marks.

4. All parts of Question paper must be answered in one place.

BL – Blooms Level

CO – Course Outcome

PART – A

		BL	CO
1.a)	How do you find the average and RMS values of a non-sinusoidal periodic waveform using Fourier coefficients?	L2	CO1
b)	What is the relationship between the trigonometric and exponential forms of a Fourier series?	L2	CO1
c)	Express the relationship between Z and Hybrid (h) parameters.	L2	CO2
d)	Why h-parameters are called as 'hybrid' parameters?	L2	CO2
e)	Distinguish between the natural response and the forced response of a circuit.	L2	CO3
f)	What is the condition for a series RLC circuit to be underdamped, overdamped and critically damped?	L2	CO3
g)	List the advantages of a three-phase system over a single-phase system.	L2	CO4
h)	How can the power factor of a balanced three-phase load be determined from the readings of two watt meters?	L2	CO4
i)	Define the cut-off frequency for a filter.	L1	CO5

j)	Draw the equivalent circuit of a typical band-pass filter.	L3	CO5
----	--	----	-----

PART - B

		BL	CO	Max. Marks
--	--	----	----	------------

UNIT-I


2	Solve the Laplace transform of the following functions: a) $f(t) = e^{-at} \sin(\omega t)$ b) $f(t) = t^2 u(t-1)$	L3	CO1	10 M
---	---	----	-----	------

OR

3	Determine the Laplace transform of the periodic sawtooth waveform.	L3	CO1	10 M
---	--	----	-----	------

UNIT-II

4	Find the z-parameters of the two-port network shown in the figure.	L3	CO2	10 M
---	--	----	-----	------

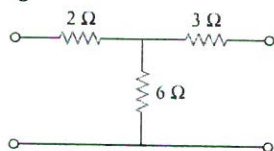

$$\begin{bmatrix} 8 & 6 \\ 6 & 3 \end{bmatrix}$$

OR

5	a) Derive the expressions for converting Y-parameters into ABCD (transmission) parameters.	L3	CO2	5 M
---	--	----	-----	-----

b)	Determine the transmission parameters for a two-port network, Given Z-parameters are $Z = \begin{bmatrix} 10 & 5 \\ 3 & 8 \end{bmatrix}$	L3	CO2	5 M
----	--	----	-----	-----

UNIT-III

6	A series RLC circuit with $R=5 \Omega$, $L=1 \text{ H}$ and $C=0.25 \mu\text{F}$ is excited by a 100 V DC source at $t=0$. Obtain the expression for the current $i(t)$ using the Laplace transform approach.	L4	CO3	10 M
---	---	----	-----	------

$$-2.5 + j2000$$

$$e^{st} [A \cos(\omega t) + B \sin(\omega t)]$$

$$0.05 e^{-2.5t} \sin 2000t$$

OR				
7	a)	Develop an expression for the step response of a series R-C circuit.	L4	CO3 5 M
	b)	Derive the general expression for the current response of a series R-L circuit excited by a sinusoidal voltage source, $V = V_m \sin(\omega t + \theta)$.	L4	CO3 5 M

UNIT-IV

8	a)	Derive the relationship between line currents and phase currents in a star-connected three-phase balanced system.	L3	CO4 5 M
	b)	The two-wattmeter method produces readings of 1500 W and 750 W when connected to a delta-connected load. Calculate the total active power, total reactive power and the power factor of the load.	L3	CO4 5 M

OR

9	A balanced star-connected load with an impedance of $(12 + j15) \Omega$ per phase is connected to a three-phase, 400 V, 50 Hz supply. Determine the line currents, power factor and total active power consumed by the load.	L4	CO4 10 M
---	--	----	----------

UNIT-V

10	a)	Design a constant-k high-pass T-section and π -section filter with a cut-off frequency of 3000 Hz and a nominal characteristic impedance of 500 Ω .	L4	CO5 5 M
	b)	Explain the characteristics of a Constant-K high-pass filter with a neat diagram.	L3	CO5 5 M

OR

11	Design a constant-k low pass filter having cut-off frequency of 4000 Hz and a nominal characteristic impedance of 500 Ω .	L4	CO5 10 M
----	--	----	----------

$$L = \frac{K}{\omega_c} = 13.27 \text{ mH}$$

$$C = \frac{1}{\omega_c K} = 0.053 \mu\text{F}$$

$$L = \frac{K}{\omega_c} = 39.79 \text{ mH}$$

$$C = \frac{1}{\omega_c K} = 1.6 \mu\text{F}$$

II B.Tech - I Semester - Regular/Supplementary Examination
November 2025

Electrical Circuit Analysis - II
(Electrical & Electronics Engineering)

1. a) - j) each question - 2M
2. a) Laplace transform of $e^{-at} \sin(\omega t)$ - 5M
 b) " " " $t^r u(t-1)$ - 5M
3. ~~5~~ sawtooth waveform & Definition - 3M
 formulae - 2M
 Laplace transform - 5M
4. z-parameter equations - 2M
 Calculation of Z_{11} - 2M
 Z_{12} - 2M
 Z_{21} - 2M
 Z_{22} - 2M
5. a) y-parameter equations - 1M
 A - 1M
 B - 1M
 C - 1M
 D - 1M
 b) value of A - 1M
 B - 2M
 C - 1M
 D - 1M
6. Circuit Diagram - 2M
 Transformed " - 2M
 KVL equation - 2M
 solution of $i(t)$ - 4M

7. a) Diagram - 2M
KVL equation - 1M
expression of $i(t)$ - 2M

b) Diagram - 2M
KVL equation - 1M
expression of $i(t)$ - 2M

8. a) Diagram - 2M
voltage relation - 2M
Current relation - 1M

b) Active power - 2M
Reactive power - 2M
power factor - 1M

9. calculation of phase voltage - 1M
 Z_{ph} - 1M

" " Line current - 3M

" " Active power - 3M

" " power factor - 2M

10. a) Formulae - 2M
Diagrams - 2M
Calculation of L & C - 1M

b) Diagrams - 1M
Any two characteristics - 4M

11. Formulae - 3M
Diagrams - 3M
Calculation of L & C - 3M

1. a) The average value of the periodic wave is

$$V_{avg} = \frac{1}{T} \int_0^T v(t) dt \quad \text{--- (11)}$$

$$v(t) = V_0 + \sum_{n=1}^{\infty} V_m \sin(n\omega t + \phi_n)$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} \quad \text{--- (11)}$$

b)

Trigonometric fourier series

$$f(t) = a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega t + b_n \sin n\omega t)$$

By substituting the cosine and sine terms

$$\cos n\omega t = \frac{e^{jn\omega t} + e^{-jn\omega t}}{2}$$

$$\sin n\omega t = \frac{e^{jn\omega t} - e^{-jn\omega t}}{2j}$$

exponential fourier series form $f(t) = \sum_{n=-\infty}^{\infty} C_n e^{jn\omega t}$

$$C_n = \frac{a_n - j b_n}{2} \quad \text{for } n > 0$$

$$C_{-n} = \frac{a_n + j b_n}{2} \quad \text{for } n > 0 \quad \text{--- 2M}$$

$$C_0 = a_0$$

c)

z terms of h

$$Z_{11} = \frac{\Delta h}{h_{22}}$$

$$Z_{12} = \frac{h_{12}}{h_{22}}$$

$$Z_{21} = \frac{-h_{21}}{h_{22}}$$

$$Z_{22} = \frac{1}{h_{22}}$$

h terms of z

$$h_{11} = \frac{Z_{11} Z_{22} - Z_{21} Z_{12}}{Z_{22}}$$

$$h_{12} = \frac{Z_{12}}{Z_{22}}$$

$$h_{21} = \frac{-Z_{21}}{Z_{22}}$$

$$h_{22} = \frac{1}{Z_{22}} \quad \text{--- 2M}$$

(OR)

d) H parameters are called hybrid because they combine parameters with mixed units and dimensionless ratios (voltage & current ratios). --- 2M

e) The main difference is that a natural response is a system behavior due to its initial conditions (e.g. capacitor & Inductor), while a forced response is the behavior caused by an external function (voltage/Current source). — 2M

- g) 1. output of a 3- ϕ system is greater than that of a 1- ϕ system.
2. In a 1- ϕ system, the instantaneous power is fluctuating in nature. However, in 3- ϕ system it is constant at all times.
3. Transmission & Distribution of a 3- ϕ system is cheaper than that of a 1- ϕ system.
4. Three-phase motors are more efficient & have high power factors than 1- ϕ motors of the same frequency.
5. 3- ϕ are self-starting where as 1- ϕ motors are not self-starting.


Note:- Allot full marks for any two advantages — 2M

h)
$$p.f = \cos(\tan^{-1}(\frac{\sqrt{3}(\omega_1 - \omega_2)}{\omega_1 + \omega_2}))$$
 — 2M

i) The cutoff frequency is the frequency at which a filter's output power drops to half of its maximum value. — 2M

(OR)
It is the point where the filter begins to significantly attenuate the input signal. It is defined as the frequency at which the output signal drops to 70.7% of its maximum amplitude.

g)

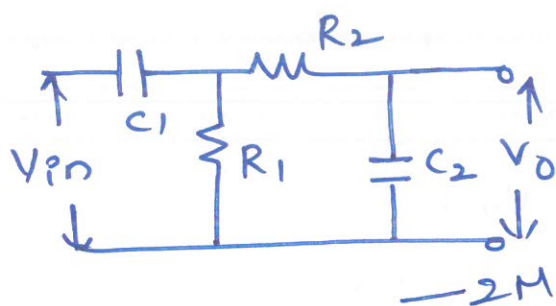

PART-B

f) Under damped $\frac{R}{2L} < \frac{1}{\sqrt{LC}}$
 over damped $\frac{R}{2L} > \frac{1}{\sqrt{LC}}$
 critically damped $\frac{R}{2L} = \frac{1}{\sqrt{LC}}$
 - 2M

UNIT-I

2. a) $f(t) = e^{-at} \sin(\omega t)$

Laplace transform of $f(t) = \sin(\omega t)$

$$= \frac{\omega}{s^2 + \omega^2}$$

By using frequency shifting theorem

$\mathcal{L}\{f(t)\} = F(s)$, then $\mathcal{L}\{e^{-at} f(t)\} = F(s+a)$

$\therefore \mathcal{L}\{e^{-at} \sin(\omega t)\} = \frac{\omega}{(s+a)^2 + \omega^2}$

(OR)

$$\mathcal{L}\{f(t)\} = \int_0^{\infty} e^{-st} f(t) dt$$

$$= \int_0^{\infty} e^{-st} e^{-at} \sin \omega t dt$$

$$= \int_0^{\infty} e^{-(s+a)t} \sin \omega t dt$$

$$= \left[\frac{e^{-(s+a)t}}{(s+a)^2 + \omega^2} (- (s+a) \sin \omega t - \omega \cos \omega t) \right]_0^{\infty}$$

$$\mathcal{L}\{e^{-at} \sin \omega t\} = \frac{\omega}{(s+a)^2 + \omega^2}$$

_____ (5M)

$$b) f(t) = t^r u(t-1)$$

t^r in terms of $(t-1)$

$$r = t-1 \quad \text{so } t = r+1$$

$$\text{Then } t^r = (r+1)^r = r^r + 2r + 1$$

Replace r with t , $g(t) = t^r + 2t + 1$

$$f(t) = (t^r + 2t + 1)u(t-1) = g(t-1)u(t-1)$$

Laplace transform of $g(t) = t^r + 2t + 1$

$$\mathcal{L}\{t^r + 2t + 1\} = \mathcal{L}\{t^r\} + 2\mathcal{L}\{t\} + \mathcal{L}\{1\}$$

$$= \frac{2}{s^3} + \frac{2}{s^2} + \frac{1}{s}$$


So,

By Apply the time-shifting property

$$\mathcal{L}\{t^r u(t-1)\} = e^{-s} g(s) = e^{-s} \left(\frac{2}{s^3} + \frac{2}{s^2} + \frac{1}{s} \right)$$

(5M)

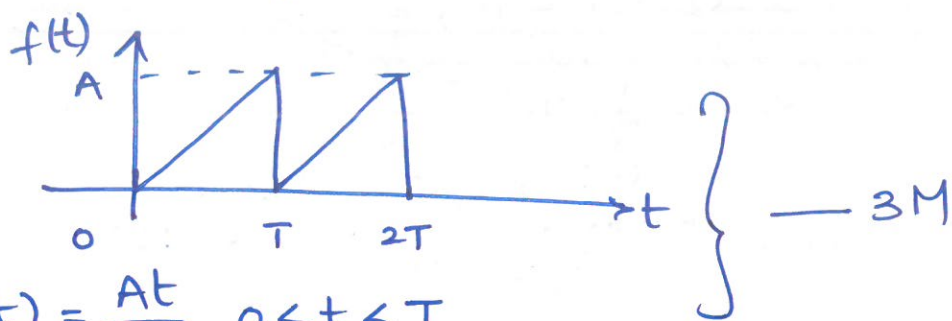3. Laplace transform of the periodic sawtooth waveform



$$\mathcal{L}\{f(t)\} = \frac{1}{1 - e^{-Ts}} \int_0^T f(t) e^{-st} dt \quad \text{--- 2M}$$

$$= \frac{1}{1 - e^{-Ts}} \int_0^T \frac{At}{T} e^{-st} dt$$

$$= \frac{1}{1 - e^{-Ts}} \cdot \frac{A}{T} \int_0^T t e^{-st} dt$$

$$= \frac{1}{1 - e^{-Ts}} \cdot \frac{A}{T} \left[\frac{t e^{-st}}{-s} \Big|_0^T - \int_0^T \frac{e^{-st}}{-s} dt \right]$$

$$= \frac{1}{1 - e^{-Ts}} \cdot \frac{A}{T} \left[\frac{t e^{-st}}{-s} \Big|_0^T - \frac{1}{s^2} e^{-st} \Big|_0^T \right]$$


$$= \frac{A}{T(1 - e^{-Ts})} \left[\frac{T e^{-sT}}{-s} + \frac{1}{s^2} - \frac{e^{-Ts}}{s^2} \right]$$

$$= \frac{A}{Ts^2} - \frac{A e^{-Ts}}{s(1 - e^{-Ts})}$$

Note: - student may consider the time period of any value and magnitude A as of any value.

Unit-II

4.

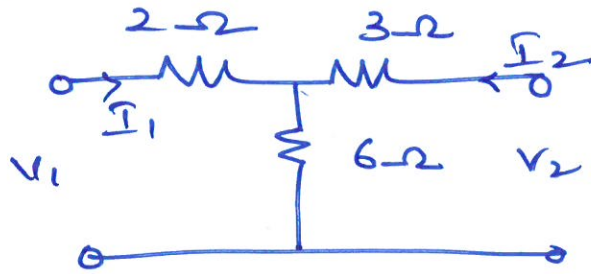

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$


when output port is open circuited $I_2 = 0$

$$R_{eq} = 2 + 6 = 8\Omega$$

$$V_1 = I_1 \times R_{eq}$$

$$Z_{11} = \frac{V_1}{I_1} = 8\Omega$$

— 2M

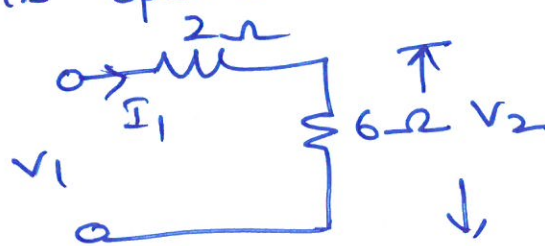


$$V_2 = 6 I_1$$

$$Z_{21} = \frac{V_2}{I_1} = 6\Omega$$

— 2M

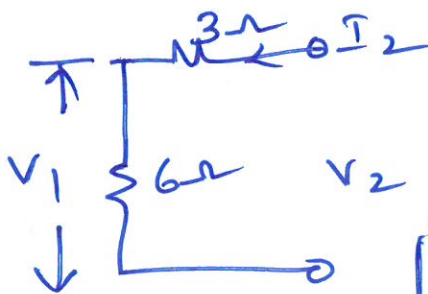when input port is open circuited $I_1 = 0$



$$R_{eq} = 3 + 6 = 9\Omega$$

$$V_2 = I_2 \times R_{eq}$$

$$Z_{22} = \frac{V_2}{I_2} = 9\Omega$$

— 2M

$$V_1 = 6 I_2$$

$$Z_{12} = \frac{V_1}{I_2} = 6\Omega$$

— 2M

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 8 & 6 \\ 6 & 9 \end{bmatrix}$$

Note:- student can also use mesh & nodal analysis to obtain Z-parameters.

5.a) Conversion of Y -parameters into ABCD parameters.

Y -parameter equations are given by

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- IM}$$

$$V_1 = \left(\frac{-Y_{22}}{Y_{21}} \right) V_2 + \left(-\frac{1}{Y_{21}} \right) (-I_2)$$

$$V_1 = \left(\frac{-Y_{22}}{Y_{21}} \right) V_2 - \left(-\frac{1}{Y_{21}} \right) I_2 \quad \text{--- (1)}$$

$$\& \quad I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- HM}$$

$$= Y_{11} \left[\left(\frac{-Y_{22}}{Y_{21}} \right) V_2 + \left(\frac{1}{Y_{21}} \right) I_2 \right] + Y_{12} V_2$$

$$I_1 = \left[\frac{-Y_{11} Y_{22} - Y_{12} Y_{21}}{Y_{21}} \right] V_2 - \left(-\frac{Y_{11}}{Y_{21}} \right) I_2$$

Comparing Equations (1) & (2) with the governing equations of ABCD parameters --- (2)

$$A = \left(\frac{-Y_{22}}{Y_{21}} \right) \quad ; \quad B = \left(-\frac{1}{Y_{21}} \right) \quad \text{--- IM}$$

$$C = \left[\frac{-Y_{11} Y_{22} - Y_{12} Y_{21}}{Y_{21}} \right] \quad ; \quad D = \left(-\frac{Y_{11}}{Y_{21}} \right) \quad \text{--- IM}$$

5.b) Given $Z = \begin{bmatrix} 10 & 5 \\ 3 & 8 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$

ABCD parameters for a two-port network

$$A = \frac{Z_{11}}{Z_{21}} = \frac{10}{3} \quad ; \quad \text{--- IM}$$


$$B = \frac{Z_{22} Z_{11} - Z_{12} Z_{21}}{Z_{21}} = \frac{8 \times 10 - 5 \times 3}{3} = \frac{65}{3} = 21.67 \, \Omega \quad \text{--- 2M}$$

$$C = \frac{1}{Z_{21}} = \frac{1}{3} \Omega \quad -1M$$


$$D = \frac{Z_{22}}{Z_{21}} = \frac{8}{3} \quad -1M$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \frac{10}{3} & \frac{65}{3} \\ \frac{1}{3} & \frac{8}{3} \end{bmatrix}$$

Unit-III

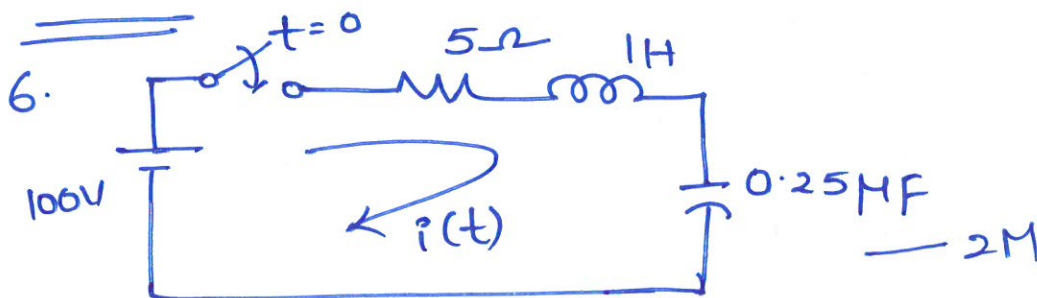

Transformed network is

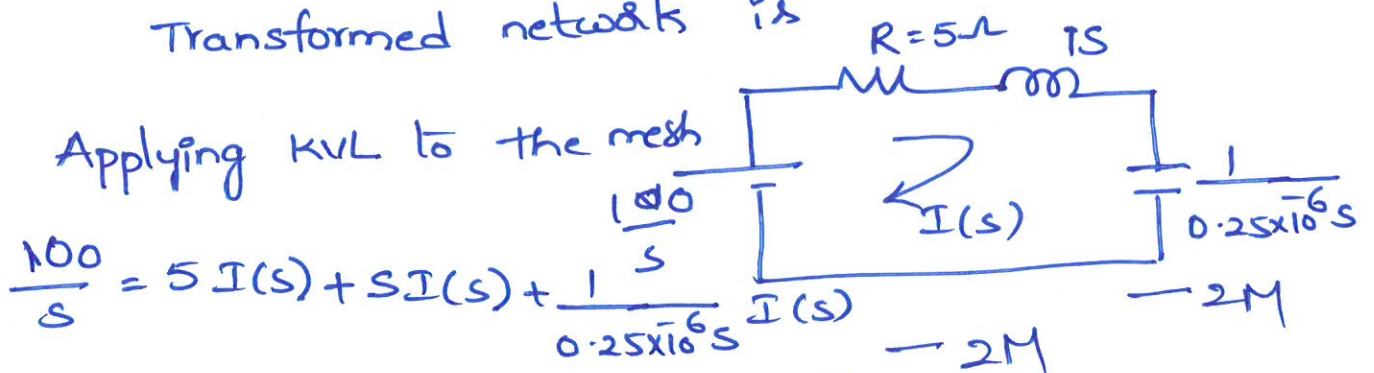

$$\frac{100}{s} = 5I(s) + sI(s) + \frac{1}{0.25 \times 10^{-6} s} I(s)$$

$$\frac{100}{s} = 5I(s) + sI(s) + \frac{4 \times 10^6}{s} I(s)$$

$$\frac{100}{s} = \frac{s^2 I(s) + 5sI(s) + 4 \times 10^6 I(s)}{s}$$

$$100 = (s^2 + 5s + 4 \times 10^6) I(s)$$

$$I(s) = \frac{100}{s^2 + 5s + 4 \times 10^6}$$

$$s^2 + 5s + 4 \times 10^6 = \frac{-5 \pm \sqrt{(5)^2 - 4(4 \times 10^6)}}{2}$$

$$= -2.5 \pm j2000 \quad \& \quad -2.5 \pm j999.99$$

The solution for this is

$$\alpha = +2.5 \quad \beta = 2000$$

$$i(t) = e^{\alpha t} (A \cos \beta t + B \sin \beta t)$$

At $t=0$; $i(0)=0$, $A=0$

$$\therefore i(t) = e^{-\alpha t} B \sin \beta t$$

$$i(t) = e^{-2.5t} B \sin 2000t$$

$$\frac{di}{dt} = B e^{-2.5t} 2000 \cos 2000t - 2.5 e^{-2.5t} B \sin 2000t$$

since the end capacitor act as short ckt

$$V = V_L = L \frac{di}{dt} = 100$$


$$\therefore \frac{di}{dt} = 100$$

$$100 = B \times 2000 \times 1$$

$$B = \frac{1}{20} = 0.05$$

$$\therefore i(t) = 0.05 e^{-2.5t} \sin 2000t \quad \text{--- 4M}$$

7.a)

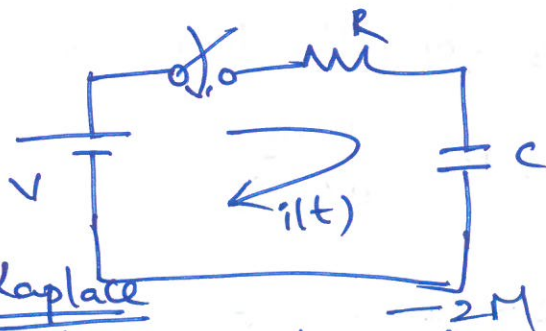

Laplace
Applying KVL to mesh
after transforming to s-domain

$$\frac{V}{s} = R I(s) + \frac{1}{Cs} I(s) \quad \text{--- 2M}$$

$$I(s) = \frac{V/s}{R + \frac{1}{Cs}}$$

$$= \frac{V/R}{s + 1/RC}$$

$$\therefore I(s) = \frac{V/R}{s + 1/RC}$$

Taking inverse Laplace transform
 $i(t) = V - (V/R) e^{-t/RC}$

Applying KVL to loop

$$Ri + \frac{1}{C} \int i dt = V \quad (1)$$

Differential

$$R \frac{di}{dt} + \frac{1}{C} i = 0$$

$$(p + \frac{1}{RC}) i = 0 \quad (2)$$

The solution to this is

$$i = i_c = C e^{-t/RC}$$

$$\text{at } t=0^+, i(0^+) = \frac{V}{R}$$


$$\therefore C = V/R$$

$$\therefore i = \frac{V}{R} e^{-t/RC} \text{ Amps.}$$

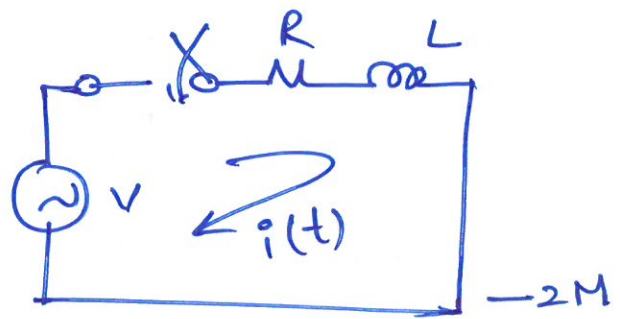7. b) $V = V_m \sin(\omega t + \theta)$

Applying KVL

$$Ri + L \frac{di}{dt} = V_m \sin(\omega t + \theta)$$



$$\frac{R}{L} i + \frac{di}{dt} = \frac{V_m}{L} \sin(\omega t + \theta)$$

$$\left(p + \frac{R}{L}\right) i = \frac{V_m}{L} \sin(\omega t + \theta) \quad \text{--- (1)}$$

$$i_c = c e^{-R/Lt} \quad \text{--- (2)}$$

$$i_p = A \cos(\omega t + \theta) + B \sin(\omega t + \theta) \quad \text{--- (3)}$$

$$\frac{di_p}{dt} \& p i_p = -A\omega \sin(\omega t + \theta) + B\omega \cos(\omega t + \theta) \quad \text{--- (4)}$$

Sub eq(3) & eq(4) in eq(1)

$$\left(-A\omega + \frac{BR}{L}\right) \sin(\omega t + \theta) + \left(B\omega + \frac{AR}{L}\right) \cos(\omega t + \theta) = \frac{V_m}{L} \sin(\omega t + \theta)$$

equating coefficients of like terms & solving

$$A = \frac{-\omega L V_m}{R^2 + \omega^2 L^2} ; B = \frac{R V_m}{R^2 + \omega^2 L^2}$$

$$\therefore i_p = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \left[-\omega L \cos(\omega t + \theta) + R \sin(\omega t + \theta) \right]$$

$$\text{Let } R = \cos \phi \text{ \& } \omega L = \sin \phi \quad \phi = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$\therefore i_p = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \left[\sin(\omega t + \theta - \tan^{-1}\left(\frac{\omega L}{R}\right)) \right]$$

The complete solution is

$$i = c e^{-(R/L)t} + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin(\omega t + \theta - \tan^{-1}\left(\frac{\omega L}{R}\right))$$

At $t=0$, $i_0=0$.

$$\therefore C = \frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin\left(\theta - \tan^{-1}\left(\frac{\omega L}{R}\right)\right)$$

$$\therefore i = e^{-(R/L)t} \left[\frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin\left(\theta - \tan^{-1}\left(\frac{\omega L}{R}\right)\right) + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin\left(\omega t + \theta - \tan^{-1}\left(\frac{\omega L}{R}\right)\right) \right] \quad \text{--- 2M}$$

8. a)


Let $V_{RN} = V_{YN} = V_{BN} = V_{ph}$

$$V_{RN} = V_{ph} \angle 0^\circ$$

$$V_{YN} = V_{ph} \angle -120^\circ$$

$$V_{BN} = V_{ph} \angle -240^\circ$$

$$V_{RY} = V_{YB} = V_{BR} = V_L$$

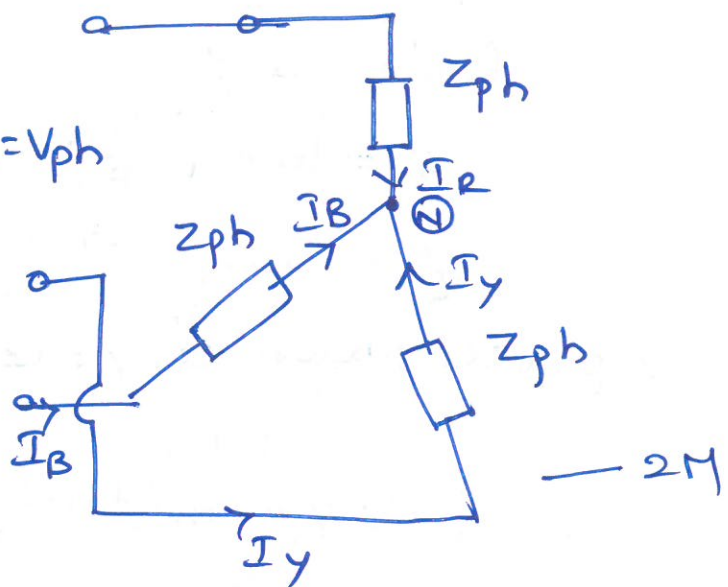

Applying KVL $V_{RY} = V_{RN} + V_{NY}$
 $= V_{ph} \angle 0^\circ - V_{ph} \angle -120^\circ$
 $= \sqrt{3} V_{ph} \angle 30^\circ$

|| $V_{YB} = V_{BR} = \sqrt{3} V_{ph} \angle 30^\circ$. --- 2M

It is clear from the above diagram that line current is equal to the phase current.

$$I_L = I_{ph}. \quad \text{--- 1M}$$

8. b) $W_1 = 1500W$ $W_2 = 750W$ delta connected load

$$\begin{aligned}\text{Total active power} &= W_1 + W_2 \\ &= 1500 + 750 \\ &= 2250W \quad \text{--- 2M}\end{aligned}$$

$$\begin{aligned}\text{Total reactive power } Q_T &= \sqrt{3}(W_1 - W_2) \\ &= \sqrt{3}(1500 - 750) \\ &= \sqrt{3}(750) \\ &= 1299.04VAR \quad \text{--- 2M}\end{aligned}$$

power factor $\cos\phi$.

$$\phi = \tan^{-1}\left(\frac{Q}{P}\right)$$

$$\phi = \tan^{-1}\left(\frac{1299.04}{2250}\right) = 30^\circ$$

power factor $\cos\phi = \cos(30^\circ) = 0.866$.

$$\begin{aligned}(\text{OR}) \\ \cos\phi &= \cos\left(\tan^{-1}\left(\frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2}\right)\right) \\ &= 0.866 \quad \text{--- 1M}\end{aligned}$$

9. $Z_{ph} = 12 + j15$ Y-connected load

phase voltage $V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 230.94 \text{ --- 1M}$

$Z_{ph} = 19.21 \angle 51.34 \text{ --- 1M}$

Line current = phase current

$$I_L = I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{230.94}{19.21} = 12.02 \angle -51.34 \text{ --- 3M}$$

Active power $P = \sqrt{3} V_L I_L \cos\phi$

$$= \sqrt{3} \times 400 \times 12.02 \times \cos(51.34)$$

$P = 5.2KW \quad \text{--- 3M}$



power factor $\cos\phi = \cos(51.34) = 0.62 \text{ --- 2M}$

10. a)

$$f_c = 3000 \text{ Hz} \quad K = 500 \Omega$$


$$L = \frac{K}{4\pi f_c} = \frac{500}{4\pi \times 3000} = 13.27 \text{ mH} \quad \left. \begin{array}{l} 1 \\ 2 \\ 3 \end{array} \right\}$$
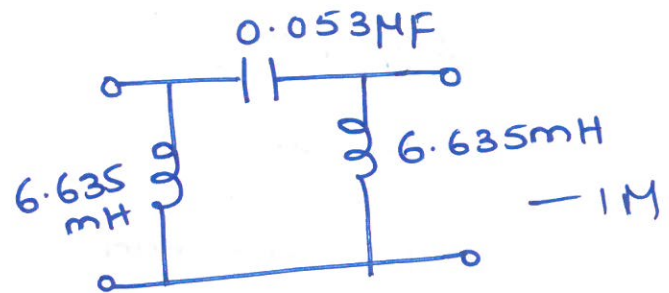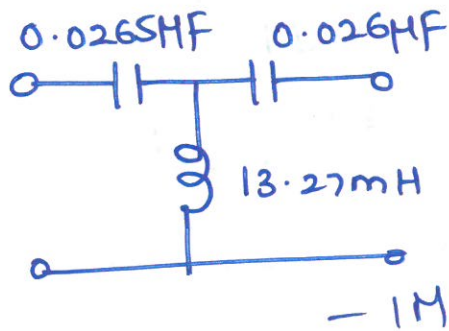
$$C = \frac{1}{4\pi f_c K} = \frac{1}{4\pi \times 3000 \times 500} = 0.053 \text{ MF}$$




10. b)

constant K-high pass filter.

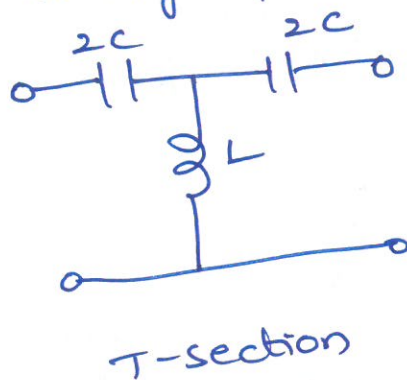

T-section

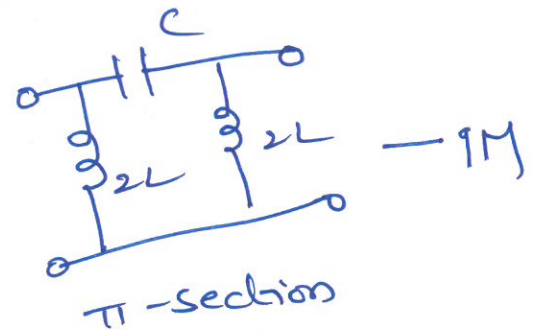

pi-section

$$Z_1 = -j \frac{1}{\omega C} = \frac{1}{j\omega C}$$

$$Z_2 = j\omega L$$

$$K = \sqrt{Z_1 Z_2} = \sqrt{\frac{L}{C}}$$

1. Nominal impedance

2. Cut-off frequency

$$\text{when } \frac{Z_1}{4Z_2} = 0 \rightarrow f = \infty$$

$$\frac{Z_1}{4Z_2} = -1 \rightarrow f_c = \frac{1}{4\pi\sqrt{LC}}$$

The pass band starts at $f = f_c$ & continues up to infinite frequency.

3. Attenuation constant:-

In pass band, $\alpha = 0$

$$\text{In stop band, } \alpha = 2 \cosh^{-1} \sqrt{\left| \frac{Z_1}{4Z_2} \right|}$$
$$= 2 \cosh^{-1} \left(\frac{f_c}{f} \right)$$

4. phase constant:-

$$\text{In pass band, } \beta = 2 \sin^{-1} \sqrt{\left| \frac{Z_1}{4Z_2} \right|}$$

$$= 2 \sin^{-1} \left(\frac{f_c}{f} \right)$$

In stop band, $\beta = \pi$

5. characteristic Impedance:-

$$Z_{0T} = K \sqrt{1 - \left(\frac{f_c}{f} \right)^2}$$


$$Z_{0\pi} = \frac{K}{\sqrt{1 - \left(\frac{f_c}{f} \right)^2}}$$

Note:- Allot full marks if student written
any two characteristics. each 2M.

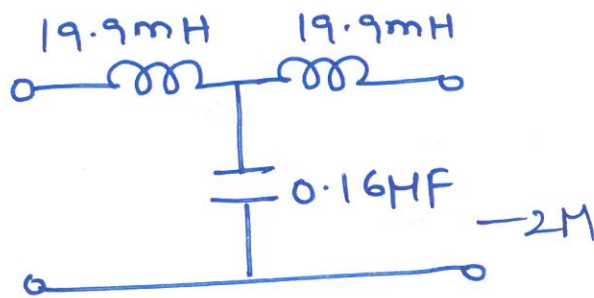
11. $f_c = 4000 \text{ Hz}$ $k = 500 \Omega$

$$L = \frac{k}{\pi f_c} = \frac{500}{\pi \times 4000} = 39.79 \text{ mH} \quad -3M$$

$$C = \frac{1}{\pi f_c k} = \frac{1}{\pi \times 4000 \times 500} = 0.16 \mu\text{F} \quad -3M$$



T-section

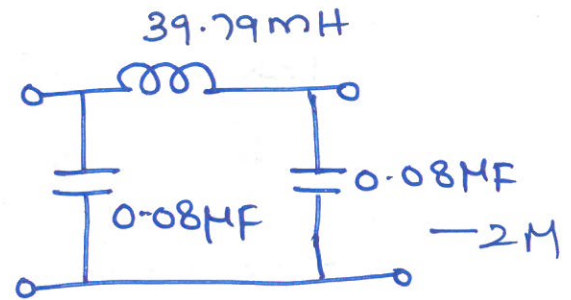

π-section

