

Code: 23EC3302

**II B.Tech - I Semester – Regular Examinations - DECEMBER 2024****SWITCHING THEORY AND LOGIC DESIGN  
(ELECTRONICS & COMMUNICATION ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

Note: 1. This question paper contains two Parts A and B.

2. Part-A contains 10 short answer questions. Each Question carries 2 Marks.

3. Part-B contains 5 essay questions with an internal choice from each unit. Each Question carries 10 marks.

4. All parts of Question paper must be answered in one place.

BL – Blooms Level

CO – Course Outcome

**PART – A**

		BL	CO
1.a)	Define Self Complimenting Code.	L1	CO1
1.b)	Simplify the following Boolean expression $F = A+B+A'B'C$ .	L2	CO3
1.c)	Given $F = xy + x'z$ . Convert this into canonical SOP form.	L2	CO3
1.d)	Realize Ex-OR gate using NAND Gates.	L3	CO2
1.e)	Draw the logic diagram of 4x1 Mux.	L2	CO2
1.f)	Write the truth table of BCD to 7-segment decoder.	L2	CO4
1.g)	Compare Latch and flip-flop.	L2	CO4
1.h)	Compare combinational and sequential circuits.	L2	CO4
1.i)	What is Mealy and Moore model?	L1	CO5
1.j)	Write the excitation table of JK flip-flop.	L1	CO5

## PART – B

			BL	CO	Max. Marks
<b>UNIT-I</b>					
2	a)	Using Hamming Code, the received message is 0001110. Find errors, if any, and give the correct message by using Even Parity.	L3	CO1	5 M
	b)	Perform BCD Subtraction for following decimal numbers: 56 - 28.	L3	CO1	5 M
<b>OR</b>					
3	a)	Realise $F = BD' + C'D' + B'D$ using NAND gates.	L2	CO2	5 M
	b)	Define Signed Binary number and explain the different compliment forms in signed numbers with example.	L2	CO1	5 M
<b>UNIT-II</b>					
4	a)	Simplify $F(A,B,C,D) = \sum m(4,5,6,7,12,13,14) + d(1,9,11,15)$ using K-map.	L3	CO3	6 M
	b)	Implement the following Boolean function $F = WY + WXY + W'XY + WX + Z$ using NAND gates.	L3	CO2	4 M
<b>OR</b>					
5	a)	Convert the given function to canonical POS form $F = (A+B)(B+C)(A+C)$	L3	CO3	5 M
	b)	Simplify the following Boolean function using K-map $F(A,B,C,D) = \prod M(1,3,4,11,12,13,14,15)$	L3	CO3	5 M

### UNIT-III

6	a)	Design BCD to Excess-3 Code Converter.	L5	CO4	5 M
	b)	Design and explain a 4-bit binary parallel Adder / Subtractor.	L4	CO4	5 M

### OR

7	a)	Realise the function $F(A, B, C, D) = \sum m(0, 1, 5, 6, 7, 10, 14)$ using an 8x1 multiplexer.	L3	CO4	5 M
	b)	Design Full adder and draw the logic diagram with help of simplified output expressions.	L4	CO4	5 M

### UNIT-IV

8	a)	Explain the operation of Master slave J-K flip flop.	L3	CO4	5 M
	b)	Explain the operation of bidirectional shift register with the help of logic diagram.	L3	CO4	5 M

### OR

9	a)	Draw and explain a 4-bit ring counter using D - flip flops	L4	CO4	5 M
	b)	Derive the Characteristic equation, Excitation table and State diagram of D-flipflop.	L3	CO4	5 M

### UNIT-V

10	a)	Design a 1011 sequence detector and draw its logic diagram.	L5	CO5	6 M
	b)	Explain State Diagram and State table.	L2	CO5	4 M

**OR**

11	a)	Using partitioning minimization procedure reduce the following state table: <table><tr><th rowspan="2">PS</th><th colspan="2">NS</th><th>Output</th></tr><tr><th>X=0</th><th>X=1</th><th>Z</th></tr><tr><td>A</td><td>D</td><td>B</td><td>1</td></tr><tr><td>B</td><td>A</td><td>E</td><td>0</td></tr><tr><td>C</td><td>A</td><td>E</td><td>1</td></tr><tr><td>D</td><td>C</td><td>A</td><td>0</td></tr><tr><td>E</td><td>F</td><td>D</td><td>0</td></tr><tr><td>F</td><td>F</td><td>D</td><td>1</td></tr></table>	PS	NS		Output	X=0	X=1	Z	A	D	B	1	B	A	E	0	C	A	E	1	D	C	A	0	E	F	D	0	F	F	D	1	L3	CO5	5 M
PS	NS			Output																																
	X=0	X=1	Z																																	
A	D	B	1																																	
B	A	E	0																																	
C	A	E	1																																	
D	C	A	0																																	
E	F	D	0																																	
F	F	D	1																																	
	b)	A sequential circuit has two JK flip-flops A and B. The flip-flop input functions are: $J_A=B$ ; $K_A= Bx$ $J_B=x$ ; $K_B=A\oplus x$ i) Draw the logic diagram of the circuit ii) Tabulate the state table iii) Draw the state diagram	L4	CO5	5 M																															